

# EE2112- Lab 1 Submission Sheet

Student Full Name: ELI Schmitt  
Laboratory Section: L02  
Laboratory TA Name: ASH FAVOR RAHMAN  
Date of submission:

## Resistance Measurements

1. Fill in Table 1 and state whether each resistor meets the manufacturer's tolerance specification. Give the reason why your fingers can't touch the resistor when measuring it. (40 pts)

Table 1: Resistance Measurements (Color Codes, Measurements, and Percent Error) [Table 1 of the lab manual]

Nominal Value	Color Code	Nominal Tolerance(%)	Measured Resistance	Percent of Error (%)	Within Manufacturer's
1.5k $\Omega$	Br G R Gold	5%	1.474k $\Omega$	0.4%	Yes
2.2k $\Omega$	R R R Gold	5%	2.165k $\Omega$	1.40%	Yes
3.3k $\Omega$	Or Or R Gold	5%	3.276k $\Omega$	0.30%	Yes
4.7k $\Omega$	Y G R Gold	5%	4.642k $\Omega$	1.2%	Yes

~~You can't~~ IF you touch the resistor you ~~can't~~ should be careful  
it is parallel with the resistor ~~change the measurement~~

TA's initials:

*Rahman*  
09/10/19

## Voltage and Current Measurements for Single-Resistor Circuit

2. Fill in Table 2 in your data sheet and compare your measured and calculated values of  $I$  and  $V$ . How does the value of  $V/I$  compare to the value you measured in Table 1? Give reasons for the similarities or differences on your data collection report. Justify your answer. (10 pts)

Table 2: Voltage and Current Measurements for Single-Resistor Circuit [Table 3 of the lab manual]

$V_s(V)$	$V_{R1}(V)$	$I_{R1}(mA)$	$\frac{V}{I} (k\Omega)$	$V_{oc}(V)$	$I_{oc}(mA)$
8	8	1.72	4.65	8	0

TA's initials:



09/10/12

## Voltage and Current Measurements for Four-Resistor Circuit

3. Theoretically in Fig. 14 which two resistors should have the same current through them? Why? (10 pts)

$R_3$  and  $R_4$ . Current does not change when two resistors are in series.

4. Fill in Table 3 in your data collection report. (40 pts)

Table 3: Voltage and Current Measurements for Four-Resistor Circuit [Table 5 of the lab manual]

R (k $\Omega$ )	V <sub>R</sub> (V)	I <sub>R</sub> (mA)	$\frac{V_R}{I_R}$ (k $\Omega$ )	Percent of Error%
1.5	3.728	<del>1.147</del> 2.486	<del>2.126</del> 1.494	0.4%
4.7	6.273	1.351	4.643	1.21%
2.2	2.489	1.147	2.170	4.36%
3.3	3.784	1.147	3.297	0.03%

TA's initials:

*Handwritten signature*

09/10/19