

# EE2112- Lab 1 Submission Sheet

Student Full Name: ELI Schmitt  
 Laboratory Section: LO 2  
 Laboratory TA Name: Asa Fiqor Rahmans  
 Date of submission:

## Resistance Measurements

1. Fill in Table 1 and state whether each resistor meets the manufacturer's tolerance specification. Give the reason why your fingers can't touch the resistor when measuring it. (40 pts)

Table 1: Resistance Measurements (Color Codes, Measurements, and Percent Error) [Table 1 of the lab manual]

Nominal Value	Color Code	Nominal Tolerance(%)	Measured Resistance	Percent of Error (%)	Within Manufacturer's
1.5k $\Omega$	Br 9 R Gold	5%	1.474k $\Omega$	0.4%	Yes
2.2k $\Omega$	R 2 R R Gold	5%	2.165k $\Omega$	1.40%	Yes
3.3k $\Omega$	Or Or R Gold	5%	3.276k $\Omega$	0.30%	Yes
4.7k $\Omega$	Y 7 R R Gold	5%	4.642k $\Omega$	1.2%	Yes

~~You can't~~ IF you touch the resistor you ~~can't~~ should be careful  
 it is parallel with the resistor ~~change the resistor~~

TA's initials:

Rahmans  
 09/10/19

## Voltage and Current Measurements for Single-Resistor Circuit

2. Fill in Table 2 in your data sheet and compare your measured and calculated values of  $I$  and  $V$ . How does the value of  $V/I$  compare to the value you measured in Table 1? Give reasons for the similarities or differences on your data collection report. Justify your answer. (10 pts)

Table 2: Voltage and Current Measurements for Single-Resistor Circuit [Table 3 of the lab manual]

$V_s(V)$	$V_{R1}(V)$	$I_{R1}(mA)$	$\frac{V}{I} (k\Omega)$	$V_{oc}(V)$	$I_{oc}(mA)$
8	8	1.72	4.65	8	0

TA's initials:



09/10/12

## Voltage and Current Measurements for Four-Resistor Circuit

3. Theoretically in Fig. 14 which two resistors should have the same current through them? Why? (10 pts)

$R_3$  and  $R_4$ . Current does not change when two resistors are in series.

4. Fill in Table 3 in your data collection report. (40 pts)

Table 3: Voltage and Current Measurements for Four-Resistor Circuit [Table 5 of the lab manual]

R (k $\Omega$ )	V <sub>R</sub> (V)	I <sub>R</sub> (mA)	$\frac{V_R}{I_R}$ (k $\Omega$ )	Percent of Error%
1.5	3.728	<del>1.147</del> 2.486	<del>2.386</del> 1.494	0.4%
4.7	6.273	1.351	4.643	1.21%
2.2	2.489	1.147	2.170	4.36%
3.3	3.784	1.147	3.297	0.03%

TA's initials:

*Handwritten signature*

09/10/19

MSO-X 3012A, MY50514804: Thu Feb 08 16:56:24 2018

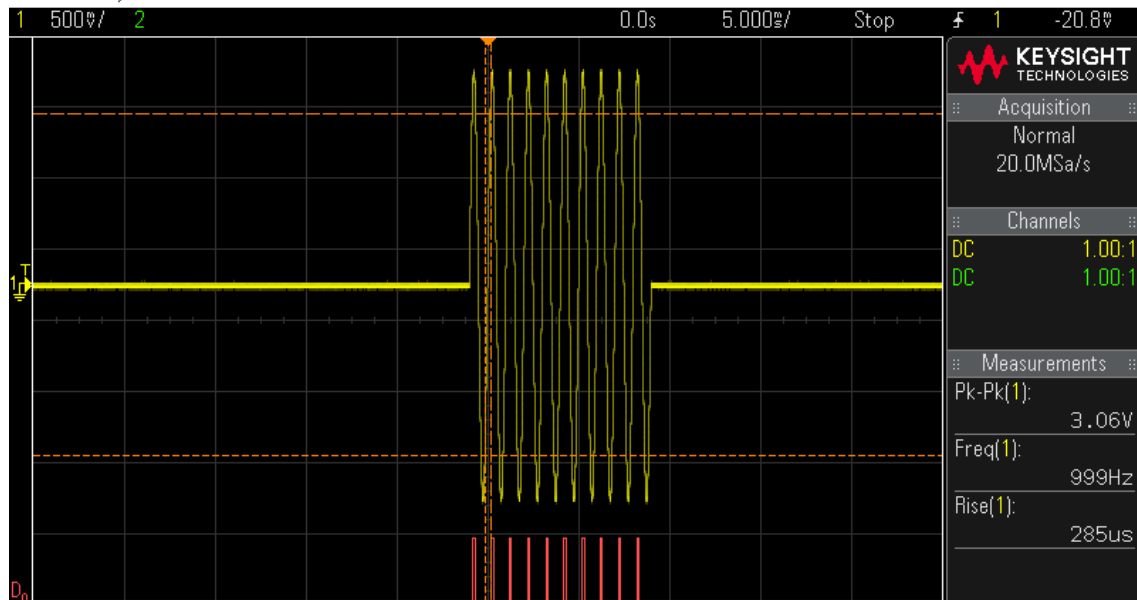


Figure 1: A picture of a capture of a 10 MHz sine wave with channel one being the wave and D0 is the digital input with the same 10 MHz wave.

MSO-X 3012A, MY50514804: Thu Feb 08 17:17:22 2018

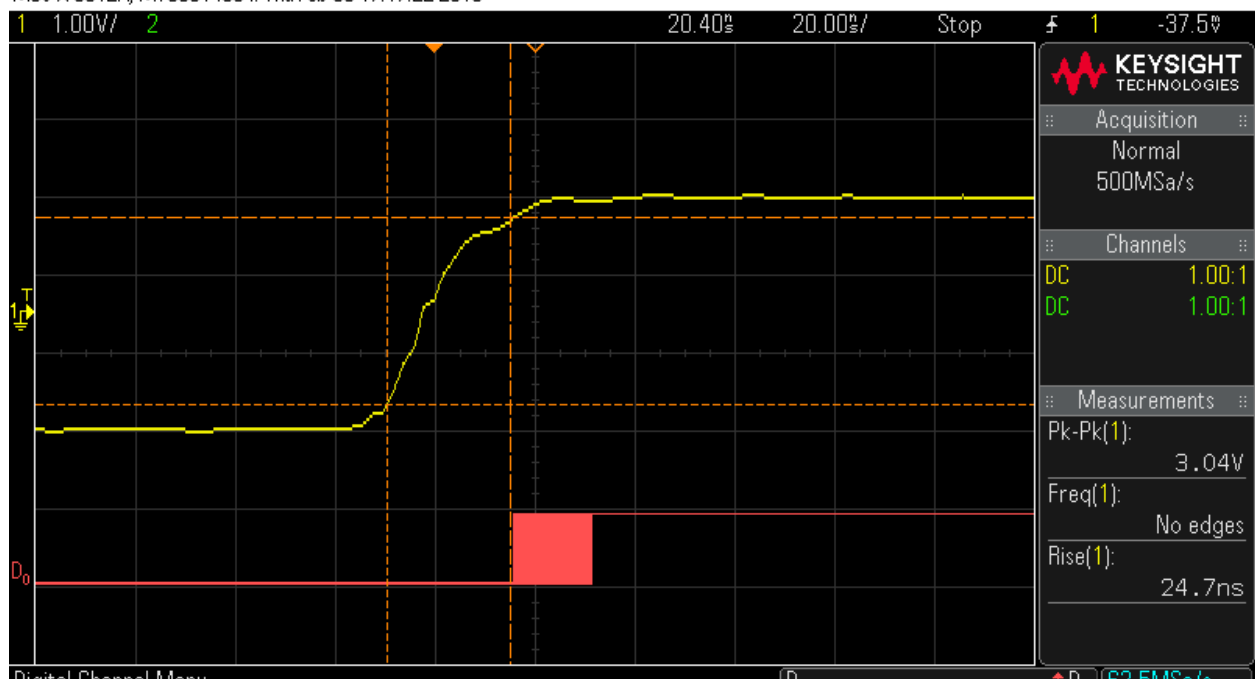


Figure 2: A Picture of a bounce from pulse generated buy a waveform generator. D0 is the digital input and Channel 1 is the pulse.

MSO-X 3012A, MY50514804: Thu Feb 08 17:30:38 2018

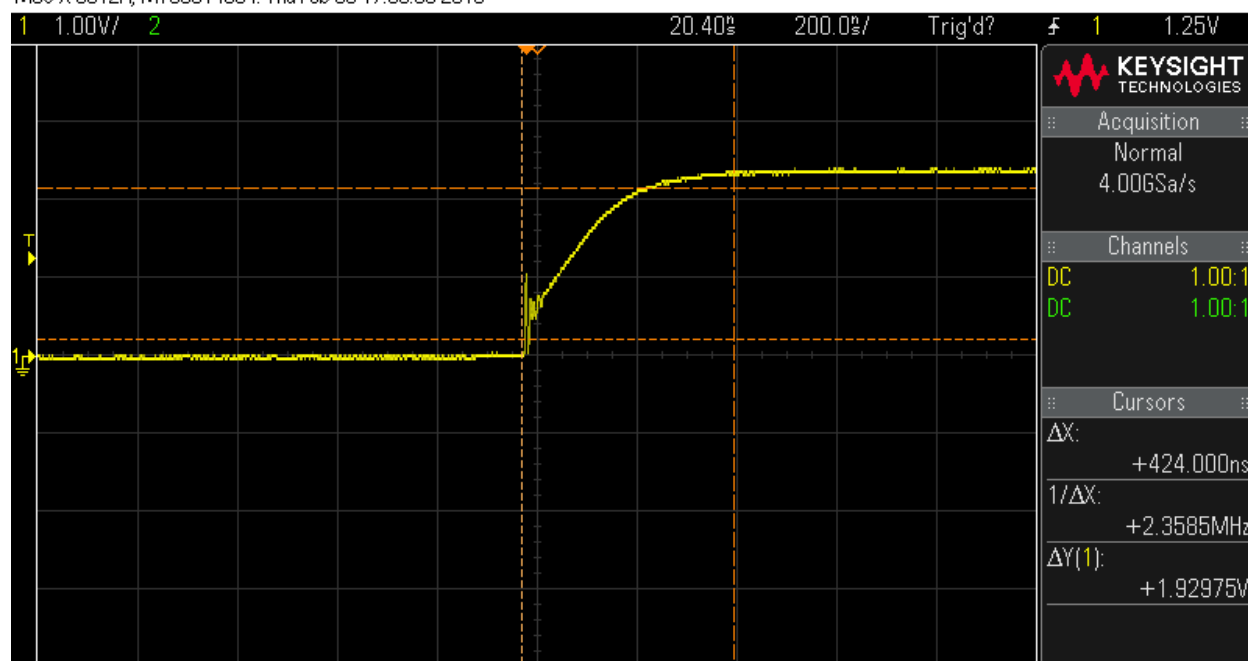


Figure 3: A picture of how a switch behaves while toggling it from high to low. The time from low to high is 424 ns.